FIGURE 1

0, 92	C=0 c=1		9,99	C=0 C=1	
00	01	16	00	00	0
01	10	L'	01	0 1	C
101	10	C'	10	0 1	(

FIGURE 2

	Wwxyz tens dies										
	10011										
	1010 +2+										
1 m/x	000 001 011 010 110 100 1017111										
00											
01	0001111111										
10	111100000										
11	00001001X										
-											
	v'w(x'x')+vw'x'+vwxyz'=+										
XX	2										
1M/	000 001 011 010 110 100 101 111										
00	0000000										
01	0000000										
11	1 1 1 1 1 1 1 1 1										
10	0 0 0 0 1 1 1 1										
-											
	VW + VW'(X)										
	AM, AM (V)										
	V(1V)										
	$V(w+w'x)$ $V(w+x) = f_2$										
	V(W+X) - T2										

FIGURE 3

Decimal	С	\$4	S3	S2	S1	W	Χ	Υ	Z
0	0	0	0	0	0	0	0	0	0
1	0	0	0	0	1	0	0	0	1
2	0	0	0	1	0	0	0	1	0
3	0	0	0	1	1	0	0	1	1
4	0	0	1	0	0	0	1	0	0
5	0	0	1	0	1	0	1	0	1
6	0	0	1	1	0	0	1	1	0
7	0	0	1	1	1	0	1	1	1
8	0	1	0	0	0	1	0	0	0
9	0	1	0	0	1	1	0	0	1
10	0	1	0	1	0	0	0	0	0
11	0	1	0	1	1	0	0	0	1
12	0	1	1	0	0	0	0	1	0
13	0	1	1	0	1	0	0	1	1
14	0	1	1	1	0	0	1	0	0
15	0	1	1	1	1	0	1	0	1
16	1	0	0	0	0	0	1	1	0
17	1	0	0	0	1	0	1	1	1
18	1	0	0	1	0	1	0	0	0
19	1	0	0	1	1	1	0	0	1
20	1	0	1	0	0	0	0	0	0
21	1	0	1	0	1	0	0	0	1
22	1	0	1	1	0	0	0	1	0
23	1	0	1	1	1	0	0	1	1
24	1	1	0	0	0	0	1	0	0
25	1	1	0	0	1	0	1	0	1
26	1	1	0	1	0	0	1	1	0
27	1	1	0	1	1	0	1	1	1
28	1	1	1	0	0	1	0	0	0
29	1	1	1	0	1	1	0	0	1
30	1	1	1	1	0	0	0	0	0